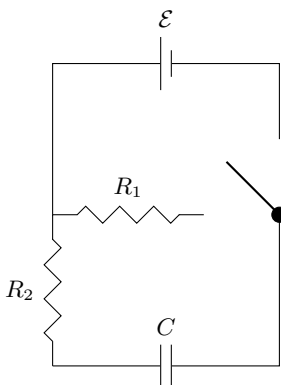


These problem starts, along with a couple released later, will be used for Quiz 2 .


Charge/Discharge

The circuit below has a switch that can be flipped to be either horizontal or vertical.




Strange capacitor

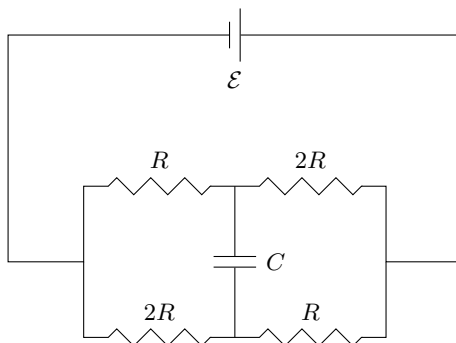The capacitor in the circuit below starts discharged. After some time, it is fully charged.



Parallel capacitors

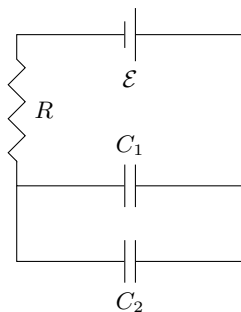The two capacitors below are wired in parallel. (Your formula sheet intentionally does not have an ‘equivalent capacitance’ formula. Perhaps you should think of one...)



General Circuits	Equivalent Resistance	Exponential Decay
$\Delta V_{\text{loop}} = 0, I_{\text{in}} = I_{\text{out}}, \Delta V_{\text{battery}} = \mathcal{E}$ $\Delta V_{\text{resistor}} = -IR, \Delta V_{\text{capacitor}} = Q/C$ $P = I\Delta V = (\Delta V)^2/R = I^2R$	$R_{\text{series}} = R_1 + R_2 + \dots$ $R_{\text{parallel}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots}$	$\frac{dy}{dt} = \lambda(y_{\text{eq}} - y)$ $\implies y = (y_0 - y_{\text{eq}})e^{-\lambda t} + y_{\text{eq}}$ $\tau = t_{1/e} = 1/\lambda = RC, t_{1/2} = \ln(2)t_{1/e}$