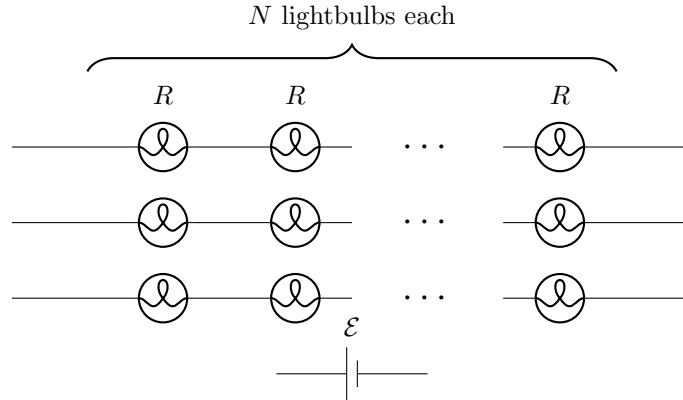



Name:

Student ID:

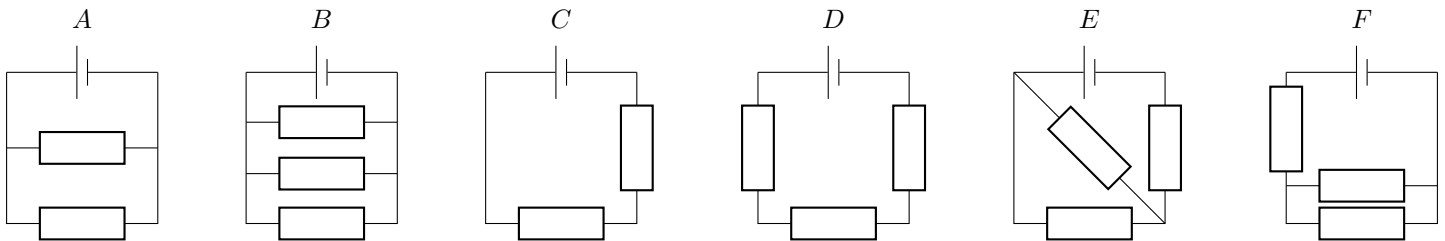Problem 1: A set of light strips is sold with three strips and one battery to power them. Each light strip consists of N identical light bulbs, each lightbulb having resistance R , attached one after another on a wire as shown in the figure below. The battery supplies a voltage \mathcal{E} . The ends of the light strips can be connected to each other, or to either end of the battery. A designer is thinking of the different ways the strips can be wired together.



Using $(\text{---}\square\text{---})$ to represent each of the strips, the designer considers the following designs, some of which don't use all three strips:



(a) For each of the following pairs of designs, compare the total power of the lightbulbs involved. (Hint: The power for a group of components can be computed using equivalent resistance, $P = (\Delta V)^2/R_{eq} = I^2 R_{eq}$)

- A and B : $P_A > P_B$ $P_A < P_B$ $P_A = P_B$ Cannot be determined
- C and D : $P_C > P_D$ $P_C < P_D$ $P_C = P_D$ Cannot be determined
- B and E : $P_B > P_E$ $P_B < P_E$ $P_B = P_E$ Cannot be determined
- E and F : $P_E > P_F$ $P_E < P_F$ $P_E = P_F$ Cannot be determined

(b) Suppose $\mathcal{E} = 120 \text{ V}$, $R = 10 \Omega$, and $N = 10$, determine the magnitude of the current through the battery in design E. (Round to 2 decimal places)


$|I_{E,\text{bat}}| = \text{[]} \text{ A}$

(c) Select all expressions that could be a magnitude of the voltage difference across an individual lightbulb in one of the designs above:

- $\frac{2\mathcal{E}}{N}$ $\frac{\mathcal{E}}{N}$ $\frac{\mathcal{E}}{2N}$ \mathcal{E} $\frac{\mathcal{E}}{2}$ $\frac{\mathcal{E}}{3}$ $\frac{\mathcal{E}}{3N}$ $\frac{2\mathcal{E}}{3N}$ $\frac{\mathcal{E}}{4N}$ $\frac{\mathcal{E}}{4}$

General Circuits	Equivalent Resistance	Exponential Decay
$\Delta V_{\text{loop}} = 0$, $I_{\text{in}} = I_{\text{out}}$, $\Delta V_{\text{battery}} = \mathcal{E}$ $\Delta V_{\text{resistor}} = -IR$, $\Delta V_{\text{capacitor}} = Q/C$ $P = I\Delta V = (\Delta V)^2/R = I^2 R$	$R_{\text{series}} = R_1 + R_2 + \dots$ $R_{\text{parallel}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots}$	$\frac{dy}{dt} = \lambda(y_{\text{eq}} - y)$ $\implies y = (y_0 - y_{\text{eq}})e^{-\lambda t} + y_{\text{eq}}$ $\tau = t_{1/e} = 1/\lambda = RC$, $t_{1/2} = \ln(2)t_{1/e}$

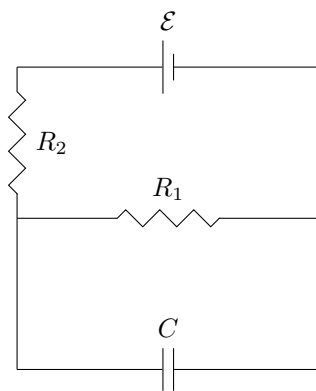Problem 2: A capacitor with capacitance C is wired 'in parallel' with a resistor R_1 . If the capacitor starts discharged, then the battery with voltage difference \mathcal{E} would charge it.



(a) At the moment when the capacitor is still discharged, what is the current through each of the components?
(Hint: Capacitor discharged means $Q = 0$.)

- Battery : 0 $\mathcal{E} \frac{R_1 R_2}{R_1 + R_2}$ $\mathcal{E} \frac{R_1 + R_2}{R_1 R_2}$ $\frac{\mathcal{E}}{R_1}$ $\frac{\mathcal{E}}{R_2}$ $\frac{\mathcal{E}}{R_1 + R_2}$
- Resistor 1 : 0 $\mathcal{E} \frac{R_1 R_2}{R_1 + R_2}$ $\mathcal{E} \frac{R_1 + R_2}{R_1 R_2}$ $\frac{\mathcal{E}}{R_1}$ $\frac{\mathcal{E}}{R_2}$ $\frac{\mathcal{E}}{R_1 + R_2}$
- Resistor 2 : 0 $\mathcal{E} \frac{R_1 R_2}{R_1 + R_2}$ $\mathcal{E} \frac{R_1 + R_2}{R_1 R_2}$ $\frac{\mathcal{E}}{R_1}$ $\frac{\mathcal{E}}{R_2}$ $\frac{\mathcal{E}}{R_1 + R_2}$
- Capacitor : 0 $\mathcal{E} \frac{R_1 R_2}{R_1 + R_2}$ $\mathcal{E} \frac{R_1 + R_2}{R_1 R_2}$ $\frac{\mathcal{E}}{R_1}$ $\frac{\mathcal{E}}{R_2}$ $\frac{\mathcal{E}}{R_1 + R_2}$

(b) After a long time, when the capacitor is fully charged, what is the magnitude of the voltage difference across each component? (Hint: Capacitor fully charged means $I_{\text{capacitor}} = 0$)


- Battery : 0 \mathcal{E} $\mathcal{E} \frac{R_1}{R_1 + R_2}$ $\mathcal{E} \frac{R_2}{R_1 + R_2}$ $\mathcal{E} \frac{R_1}{R_2}$ $\mathcal{E} \frac{R_2}{R_1}$
- Resistor 1 : 0 \mathcal{E} $\mathcal{E} \frac{R_1}{R_1 + R_2}$ $\mathcal{E} \frac{R_2}{R_1 + R_2}$ $\mathcal{E} \frac{R_1}{R_2}$ $\mathcal{E} \frac{R_2}{R_1}$
- Resistor 2 : 0 \mathcal{E} $\mathcal{E} \frac{R_1}{R_1 + R_2}$ $\mathcal{E} \frac{R_2}{R_1 + R_2}$ $\mathcal{E} \frac{R_1}{R_2}$ $\mathcal{E} \frac{R_2}{R_1}$
- Capacitor : 0 \mathcal{E} $\mathcal{E} \frac{R_1}{R_1 + R_2}$ $\mathcal{E} \frac{R_2}{R_1 + R_2}$ $\mathcal{E} \frac{R_1}{R_2}$ $\mathcal{E} \frac{R_2}{R_1}$

(c) Suppose $\mathcal{E} = 120 \text{ V}$, $R_1 = 10 \text{ } \Omega$, $R_2 = 10 \text{ } \Omega$, and $C = 5 \text{ F}$.
What is the half-life corresponding to the charging process? (Round to two decimal places)

$$t_{1/2} = \boxed{} \text{ s}$$

(d) For the graph below, the horizontal axis denotes time, with the capacitor discharged at $t = 0$. Which of the following quantities could be the ones plotted on the vertical axis?

- $|\Delta V_{\text{battery}}|$ $|I_{\text{battery}}|$
- $|\Delta V_{R_1}|$ $|I_{R_1}|$
- $|\Delta V_{R_2}|$ $|I_{R_2}|$
- $|\Delta V_{\text{capacitor}}|$ $|I_{\text{capacitor}}|$

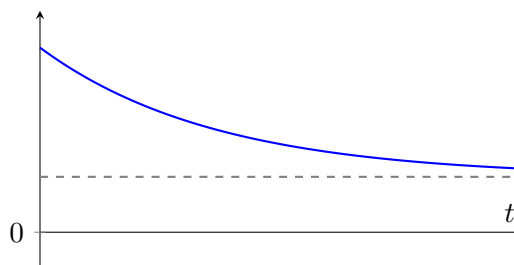

General Circuits	Equivalent Resistance	Exponential Decay
$\Delta V_{\text{loop}} = 0$, $I_{\text{in}} = I_{\text{out}}$, $\Delta V_{\text{battery}} = \mathcal{E}$ $\Delta V_{\text{resistor}} = -IR$, $\Delta V_{\text{capacitor}} = Q/C$ $P = I\Delta V = (\Delta V)^2/R = I^2 R$	$R_{\text{series}} = R_1 + R_2 + \dots$ $R_{\text{parallel}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots}$	$\frac{dy}{dt} = \lambda(y_{\text{eq}} - y)$ $\implies y = (y_0 - y_{\text{eq}})e^{-\lambda t} + y_{\text{eq}}$ $\tau = t_{1/e} = 1/\lambda = RC$, $t_{1/2} = \ln(2)t_{1/e}$